

**SUBJECT CODE NO:- P-100**  
**FACULTY OF ENGINEERING AND TECHNOLOGY**  
**S.E.(CSE/IT) Examination MAY/JUNE-2016**  
**Digital Electronics**  
**(Revised)**

[Time:Three Hours]


[Max Marks:80]

“Please check whether you have got the right question paper.”

- N.B
- i) Q.No.1 from section A and Q.No.6 from section B are compulsory, solve any two questions from remaining, from each section.
  - ii) Figures to the right indicate full marks.
  - iii) Assume suitable data, wherever necessary.

Section A

 - Q.1 Solve **any five** 10
- a) Design Boolean expression of y for the given logic diagram



- b) Reduce following using Boolean algebra  
 $Y = F(A, B, C) = \sum m(0, 1, 3, 5)$
  - c) Construct truth table for 4-input AND gate.
  - d) Draw 4-variable K-map.
  - e) What is PAL.
  - f) Convert following SOP expression to POS form  
 $F = \sum m(0, 1, 5, 6, 8, 9, 11, 13) + \sum d(7, 10, 12)$
  - g) Draw the logic symbol of clocked JK-FF write its truth table.
  - h) Explain encoder with example.
- Q.2 a) Minimize the following using Quine Mc-cluskey method 08  
 $F = \pi N(1, 2, 3, 8, 9, 10, 11, 14) . \pi D(7, 15)$
- b) Design 2-bit digital comparator. 07
- Q.3 a) What is digital signal? Explain different characteristics of digital signal. 07  
 b) Implement following Boolean expression using BCD to decimal decoder & NAND gates only 08
- i)  $F = \sum m(0, 2, 3, 5, 7)$
  - ii)  $F = \sum m(1, 3, 4, 6, 7)$
  - iii)  $F = \sum m(0, 2, 4, 5, 6, 7)$

- Q.4 a) Design 10 bit even parity generator. 08  
 b) Compare combinational & sequential circuits. 07
- Q.5 a) Design a combinational logic circuit that accepts a 4-bit binary number & output is 1, it is an even number 07  
 b) Design 16:1 MUX using 4:1 multiplexer only Explain its working. 08

Section B

- Q.6 Solve **any Five** 10
- Enlist types of shift register.
  - Draw & explain NAND implementation of 1-bit memory cell
  - Draw logic diagram for 4-bit SISO register.
  - What is counter?
  - How many flip-flops are needed to design following counter?
    - MOD-16
    - MOD-10
  - Draw block diagram of DAC.
  - Write applications of ADC.
  - Draw the diagram of left shift register.
- Q.7 a) Explain working of universal shift register IC 7495 07  
 b) Explain binary weighted register D to A convertor 08
- Q.8 a) Design synchronous decode counter using T-type flip-flop 08  
 b) Explain working of dual / slope ADC. 07
- Q.9 a) Compare synchronous and Asynchronous counter. 08  
 b) Explain PIPO shift register IC 74198. 07
- Q.10 a) Explain application of ADC & DAC. 07  
 b) Design synchronous JK counter giving the following sequence 08

