Total No. of Printed Pages:1

SUBJECT CODE NO:- P-8205 FACULTY OF ENGINEERING AND TECHNOLOGY M.E.(Electrical Power Systems) Examination MAY/JUNE-2016 HVDC Transmission (Revised)

[Time: Three Hours] [Max Marks:8			
N.B		"Please check whether you have got the right question paper." i) Solve <u>any two</u> questions from each section. ii) Assume suitable data wherever necessary. Section A	
Q.1		Explain with neat diagram the terminal equipment at the converter station. Explain in detail the operation and analysis of twelve pulse converter.	08 12
Q.2		Explain the converter bridge characteristics in detail. Explain the converter control characteristics in detail.	10 10
Q.3	-	Explain IPC and EPC schemes for firing angle control in detail. Explain the sources of harmonics and their adverse effects in HVDC system.	10 10
Q.4		Explain current and extinction angle control in HVDC system. What are the different types of dc filters? Explain the criteria of design for DC filters.	10 10
		Section B	
Q.5	-	Explain the different configurations of MTDC system. Explain the current margin control method in MTDC system.	08 12
Q.6	-	Explain a simplified continuous time model and discrete time model for the converter. Explain the modeling of DC network.	12 08
Q.7		Explain converter faults in detail. Explain the causes of over voltages in the converter station in detail.	10 10
Q.8	Write i. ii. iii.	short notes on HVDC system simulation Advantages and problems associated with earth and sea returns Insulation co-ordination	18