

SUBJECT CODE:- 230
FACULTY OF ENGINEERING AND TECHNOLOGY
S.E. (EEP/EE/EEE) Examination Nov/Dec 2015
Analog & Digital Circuits
(Revised)

[Time: Three Hours]

[Max. Marks: 80]

“Please check whether you have got the right question paper.”

N.B i) Q.No.1 and Q.No.6 are compulsory.

ii) Solve any two questions from remaining for each section.

Section A

- | | | |
|-----------|---|----------|
| Q.1 | Solve any five from following | 10 |
| | <ul style="list-style-type: none"> a. $(1010101)_2 = (?)_{16}$ b. Find 2's complement of $(11001100)_2$ c. Convert following from gray to binary. (110110) d. $(1010111)_2 + (110011)_2 = ?$ e. Explain AND & OR gate. f. $(134)_{10} = (?)_8$ | |
| Q.2 | <ul style="list-style-type: none"> a) Construct AND, OR & NOT logic using NAND gate. b) Explain the working of multiplexer | 08
07 |
| Q.3 | Simplify following equation using K map. | 15 |
| | <ul style="list-style-type: none"> a. $Y = BCD + \overline{ACD} + \overline{ABC} + \overline{ABD}$ b. $Y = \overline{BCD} + BCD + \overline{BCD} + \overline{BCD}$ c. $Y = ABCD + \overline{ABC} \overline{D}$ | |
| Q.4 | <ul style="list-style-type: none"> a) Explain memory devices in detail b) Differentiate SOP and POS | 08
07 |
| Q.5 | <ul style="list-style-type: none"> a) Explain ring counter b) Explain Master –slave J K flip-flop in detail. | 08
07 |
| Section-B | | |
| Q.6 | Solve any five from following | 10 |
| | <ul style="list-style-type: none"> a) Define load line b) Draw symbol of PNP and NPN BJT. c) Define forward active mode/biasing/cut off mode BJT d) Define avalanche breakdown e) Define current gain/voltage gain of BJT f) Draw pin diagram of IC555/Slew rate of opamp/CMRR/Pin diagram of IC741 | |
| Q.7 | <ul style="list-style-type: none"> a) Explain ratings of BJT b) Explain common emitter configuration of BJT | 08
07 |
| Q.8 | <ul style="list-style-type: none"> a) Explain Op-Amp parameter in detail b) Explain Astable multivibrator using IC55 | 08
07 |

- Q.9
- a) An op Amp has CMRR of 90dB. If its differential voltage gain is 30000 calculate common mode gain 05
 - b) A certain transistor has $\alpha = 0.98, I_{CO} = 5\mu A$ and $I_B = 100\mu A$. Find the values of collector and emitter currents. 05
 - c) Explain inverting amplifier 05
- Q.10 Write a short note on any three 15
- a. Schmitt trigger
 - b. LM 317
 - c. First order high pass filter
 - d. FET.