

SUBJECT CODE:- 124
FACULTY OF ENGINEERING AND TECHNOLOGY
S.E. (EEP/EE/EEE) Examination Nov/Dec 2015
Network Analysis
(Revised)

[Time: Three Hours]


[Max. Marks: 80]

“Please check whether you have got the right question paper.”

- N.B
- i) Use suitable data if required.
 - ii) Q.No.1 from section A and Q.No.6 from section B are compulsory.
 - iii) Solve any two questions from remaining questions from each section A and B.

Section- A

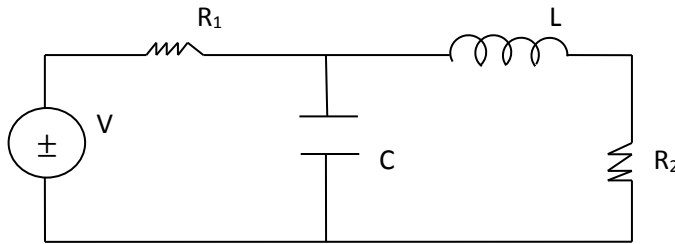- Q.1 Solve any five 10
- i) Define lumped and distributed network.
 - ii) Find the Laplace transform of unit step function.
 - iii) State superposition theorem and its application.
 - iv) Enlist the applications of Laplace transform.
 - v) Draw the voltage control voltage source and voltage control current source.
 - vi) Write the differential equation for the series RLC circuit.
 - vii) Define convolution integral
 - viii) Draw the dual of the network



- Q.2 A Find the input impedance for the circuit shown in fig.2 05

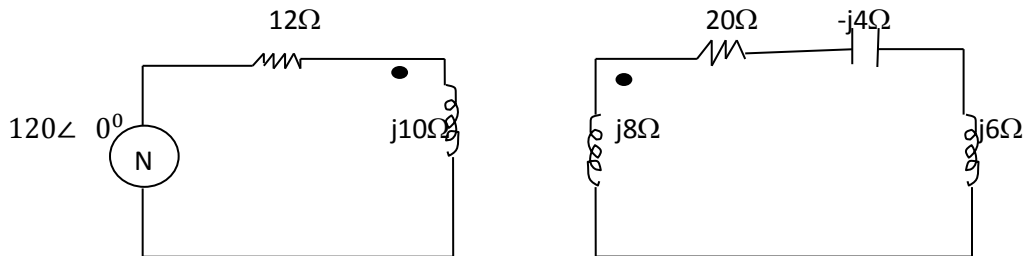


Fig.2

- B Find the current in various branches in the network the concept of super mesh in figure 3. 05

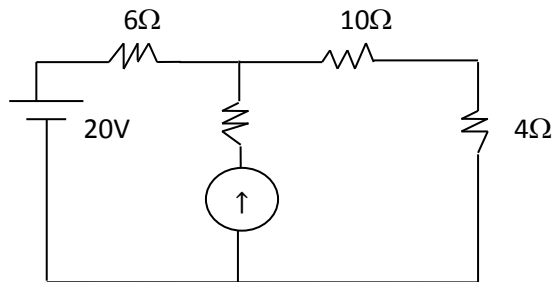


Fig.3

C In the network of figure 4 find the impedance as seen from terminals A & B if $Z_L = 10j \Omega$ in figure 4

05

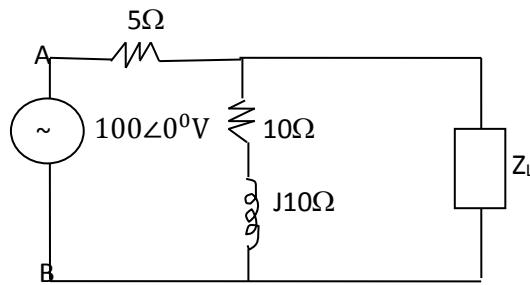


Figure 4

Q.3 A Define coupled circuits. Explain in detail the dot convention for coupled circuits.

05

B Explain the concept of source transformation in the analysis of the electrical networks.

05

C Find the voltage of nodes 1 and 2 in the network of figure 5

05

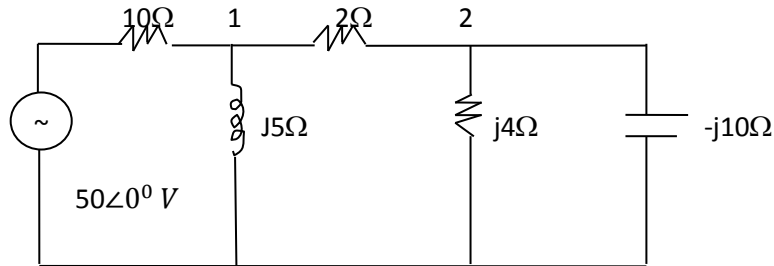


Fig.5

Q.4 A In the circuit of figure 6 the initial current is zero. Find the source current after closing of switch s.

05

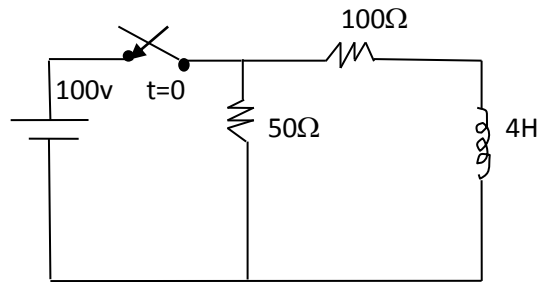


Fig.6

B For the circuit shown in fig 7 the switch is closed at $t=0$ find $i(0^+)$, $\frac{di(0^+)}{dt}$, $\frac{d^2i(0^+)}{dt^2}$

05

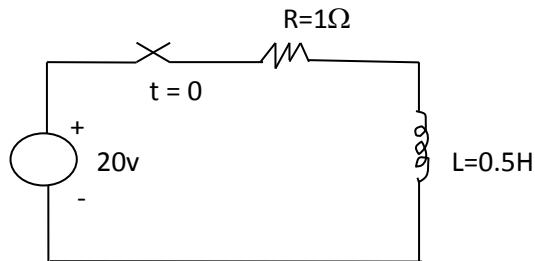


Fig.7

C State and explain reciprocity theorem

05

- Q.5 A An RC series has $R=2\Omega$ and $c=0.25f$ find current response if the during voltage is step voltage $\alpha u(t-3)$ 05
 B An impulse voltage $10 \delta(t)$ is applied to a series RC circuit having $R=2\Omega$ and $c=0.5f$. find 05
 a) Time constant b) $i(t)$ c) $i(t)$ at $t=0$ and $t=\infty$
 C The current through a $2f$ capacitor is given by the following 5 domain equation. 05
 $Z(s) = \frac{24(s+1)(s+3)}{(s+2)(s+4)(s+5)}$. Find voltage across the capacitor

Section- B

- Q.6 Solve any five 10
 i) Draw the i) T-network ii) Lattice network
 ii) What is Fourier series
 iii) State the z parameter of two port network
 iv) write y parameters in terms of z parameters
 v) A function is given by
 $P(s) = \frac{2s}{s^2+4}$ draw its pole zero plot.
 vi) Differentiate between one port and two port networks
 vii) What is s domain networks?
 viii) Obtain the s domain equation of series RL circuit with no initial current?

- Q.7 A Find the h parameters for the networks. 05


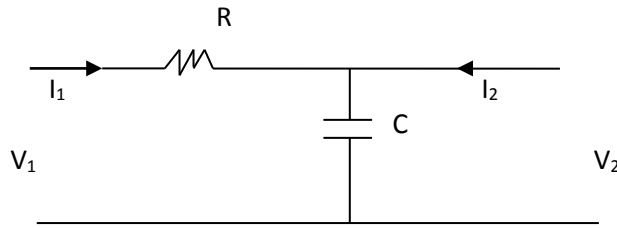



Figure .8

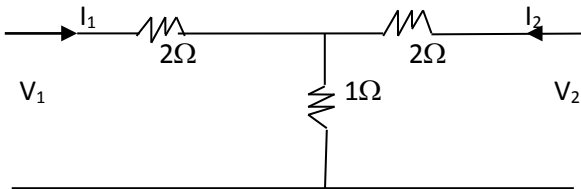- B Find z parameters for the circuit in figure 9. 05



- C What is mean by poles and zeros of a network function? 05

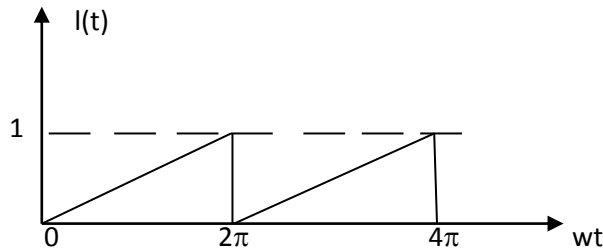- Q.8 A Find the exponential Fourier series of the given waveform in fig 10 05



- B Write short note on half wave symmetry 05
 C A coil draws 5 amps when connected to 100v 50Hz supply. The resistance of the coil is 5Ω . Determine 05

- 1) Inductance of the coil 2) Real power reactive power, appetent power of the coil.

Q.9 A The current of the following waveform is passed through 5Ω resistance. Find power consumed (Fig.11) 05

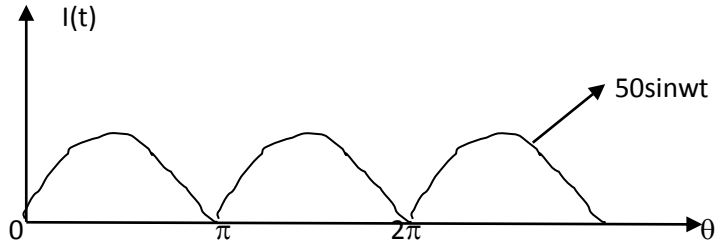


Fig.11

B Obtain the transmission parameters for the circuit shown in figure 12 05

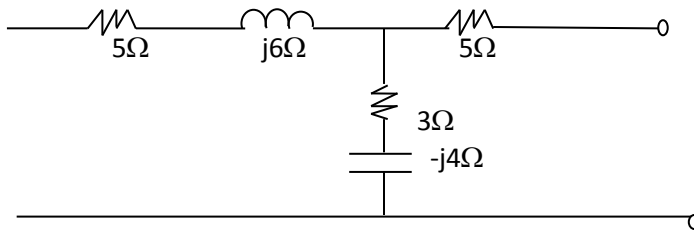


Fig.12

C Explain different types of inter connection of two ports. 05

Q.10A Obtain the transform impedance $z(s)$ of the network $z(s) = \frac{V(s)}{Z(s)}$ with zew initial condition, transform the network into s-domain (fig.13) 05

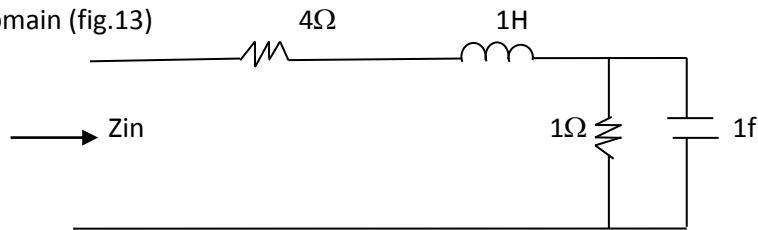


Figure 13

B Explain necessary conditions for transfer functions. 05

C For the given network function? Draw pole zew plot and obtain time response $u(t)$ 05

$$Z(s) = \frac{2s}{(s + 1)(s + 2)}$$