


Q.2

a) Explain in detail mesh analysis with an example.

05

b) Find the voltage V_a & V_b in the network of fig1. Using Nodal analysis.

05

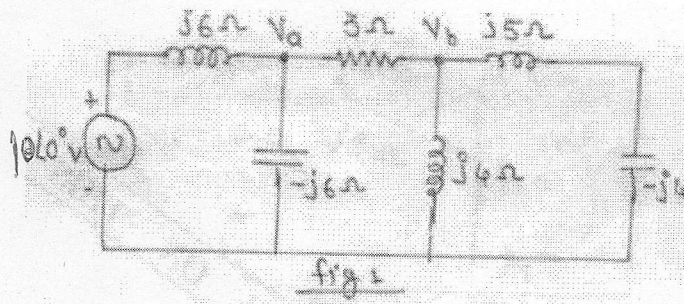

2017

- c) Determine the voltage across the $(r+j5)\Omega$ impedance for the network shown in fig 2. Using 05 superposition theorem.

