

SUBJECT CODE NO:- P-237
FACULTY OF ENGINEERING AND TECHNOLOGY
T.E.(EEP/EE/EEE) Examination May/June 2017
Power Electronics
(Revised)

[Time: Three Hours]

[Max.Marks:80]

Please check whether you have got the right question paper.

N.B

- i) Q.No.1 and Q.No.6 are compulsory.
- ii) Solve any two questions from remaining in each section
- iii) Assume suitable data it required
- iv) Draw appropriate waveforms it required

Section A

- Q.1 Solve any five 10
- a) Which PNP device is describe the following statement
 - i) Can be turned "on" or "off" at either gate
 - ii) Can be turned "on" by negative pulse
 - iii) A unilateral device turned "off" by a negative gate signal
 - iv) Can be turned "off" by reducing current by I_H .
 - b) Draw the output characteristics of n channel enhancement MOSFET
 - c) What is difference between non-punch through. IGBT_s and punch through IGBT_s
 - d) Draw the switching characters of GTO
 - e) Define the term gate recovery time
 - f) Compare IGBT and MUSFET
 - g) What is the lowest harmonic frequency present in dc output of six pulse converter
 - h) What is circuit turn off" time?
- Q.2 07
- a) What is freewheeling diode? What are its functions?
- 08
- b) Explain with near circuit & wave form the operation of single phase full controlled rectifier with inductive load
- Q.3 08
- a) A three phase half wave controlled rectifier supplying a constant load current of 30A, operated from three phase 400V (line) supply. Find the average load voltage at firing angle 45° . What value of current & peak reverse voltage rating will the thyristor require
- 07
- b) Explain the operation of 3-ph half controlled converter with RL load
- Q.4 08
- a) Draw V-I characteristics of SCR & explain the effect of gate current variation on the V-I characteristics
- 07
- b) A single phase full controlled bridge converter supplies an inductive load supply voltage is 230v/50Hz firing angle is $\pi/3$. As some that the output current is continuous & ripple free and is equal of 15amp Determine
 - (i) Average output voltage
 - (ii) Input PF
 - (iii) Fundamental PF
 - (iv) Average & rms values of SCR current
- Q.5 08
- a) What is dual converter? Explain the basic principle of operation of ideal dual converter
- 07
- b) A simple phase semi converter? Operating from a simple phase 220V, 50Hz, supply. The RLE load with

R= 5Ω, L = 10MH , & E = 100V is connected to the output of converter. Find the average value of load current for a firing angle of 45° for continuous conduction. Draw the output voltage waveforms and indicate the conducting periods of devices

Section B

- Q.6 Solve any five 10
- What is chopper? Draw the circuit diagram of step up chopper
 - A chopper operating on TRC at a frequency of 5KHz on a 200V dc supply If low voltage is 40% of supply voltage, find conduction & blocking period of SCR in each cycle
 - What is inverter? What are the different types of investors?
 - What is different between 180° and 120° mode of operation of 3 phase inverters?
 - What are the specifications of power supplies used in industrial applications?
 - What is SMPs?
 - What is the difference between fly back and forward converter?
 - What is duty ratio of chopper?
- Q.7 a) Prove that the average output voltage of step up chopper is given by 07

$$V_0 = \frac{V_{dc}}{1-\alpha}$$

Where Vdc – supply (dc) voltage
- α- duty ratio

- b) A chopper circuit supplied from 80v dc battery, supplies a R-L load with L = 40MH and R = 6Ω. The load has a freewheeling diode across it. It is required to vary to load current between 10A & 12A. Calculate the time ratio of chopper? 08
- Q.8 a) What are the draw backs of square wave inverter? What are the techniques used to overcome the draw backs of square wave inverter? 07
- b) Explain with neat circuit diagram & wave form the operation of single phase half bridge VSI with R-L load 08
- Q.9 a) Explain with neat circuit & waveform the operating modes of buck converter. 07
- b) What is cyclo converter? Explain the basic principle of operating of a cyclo converter 08
- Q.10 a) A single phase half wave AC- AC voltage controller supplying a resistive load. Prove that the average load voltage is given by 07

$$V_{0av} = \frac{V_m}{\alpha\pi} (\cos \alpha - 1)$$

- b) A single phase full bridge inverter is operated from a 24 v battery and is supplying a resistive load of 5 ohm Determine 08
- Fundamental output volt
 - fundamental output power
 - switch rating's