

“Please check whether you have got the right question paper.”

- i) Question No. 1 and Question No 6 are compulsory
- ii) Attempt from each section any two questions from the remaining questions.
- iii) Assume suitable data wherever necessary.

SECTION A

- Q.1 Solve any five questions 10
- a) What is impedance and reactance diagram?
 - b) What are the factors that need to be omitted for an impedance diagram to reduce it to a reactance diagram?
 - c) What is bus admittance matrix?
 - d) What is a bus?
 - e) What are sequence impedance and sequence network?
 - f) A generator rated at 50 MVA, 11KV, has a reactance of 25%. Calculate its per unit reactance **for a box of 100 MVA, 10KV**
 - g) Define the voltage controlled bus.
 - h) Write the expression for complex power injected to a bus. Specific the terms
- Q.2 a) For power system shown in fig.1. Convert the system to base of 100 MVA, 200 KV in 50Ω line. Neglect the resistance. The rating are 08
- Gen: 40 MVA, 25 KV, $x^{11} = 20\%$
 - Motor: 50 MVA, 11KV, $x^{11} = 30\%$
 - Y-Y transformer: 40 MVA, 33/220 KV, $x=15\%$
 - Y-A transformer: 30 MVA, 11/220KV, $x=15\%$

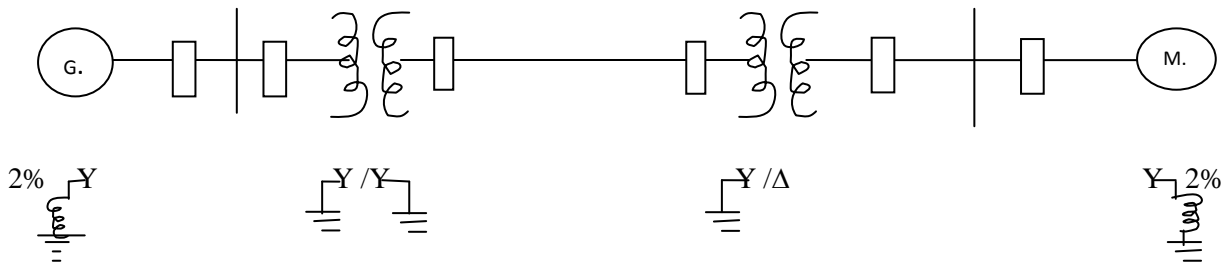


Fig.1

- b) Prove the p.u impedance of a 1φ transformer is same whether computed from primary or secondary side 07
- Q.3 a) Explain formation of network matrices lay singular transformation of Y-bus 08
- b) For the power system as shown in fig.2 obtain A, \hat{A} and K . 07

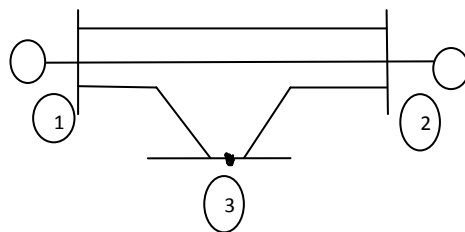


Fig.2

- Q.4 a) Discuss the significance of load flow solution in power system analysis 07

- b) For the power system show below compute Y_{BUS} and Bus voltage upto one iteration using Gauss seidel method for figure.3 08

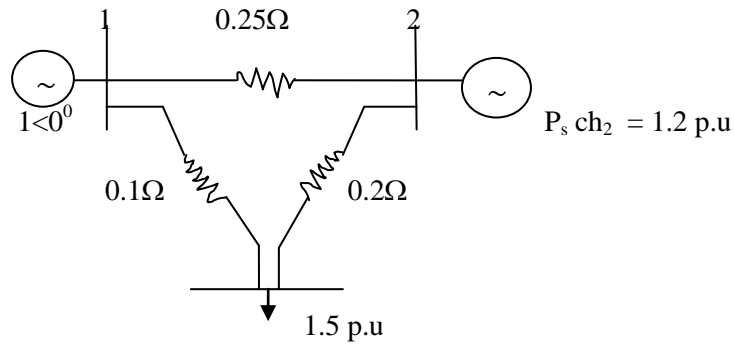


Fig.3

- Q.5 a) Explain the procedure of fast decoupled load flow method. 08
 b) Explain the selection of circuit breakers 07

SECTION B

- Q.6 Solve any five question of the following 10


- What is the need for voltage control in a power system?
- Name the main difference in representation of power system for load flow and short circuit studies
- What is need of short circuit analysis?
- What is meant by doubling effect?
- What are main factors to be considered while selection of circuit breaker?
- Why the circuit breaker interrupting current is asymmetrical?
- Name the fault in which zero sequence current do not flow and define positive sequence impedance
- How is the convergence of N.R method speeded up?

- Q.7 a) Explain the sequence impedance and network of transmission line 08

- b) Determine the symmetrical components of three voltages 07
 $V_a = 225 \angle 0^\circ$, $V_b = 225 \angle 240^\circ$ & $V_c = 225 \angle 110^\circ$

- Q.8 a) Explain the Z_{BUS} building for Type 1 & Type 3 modification 08

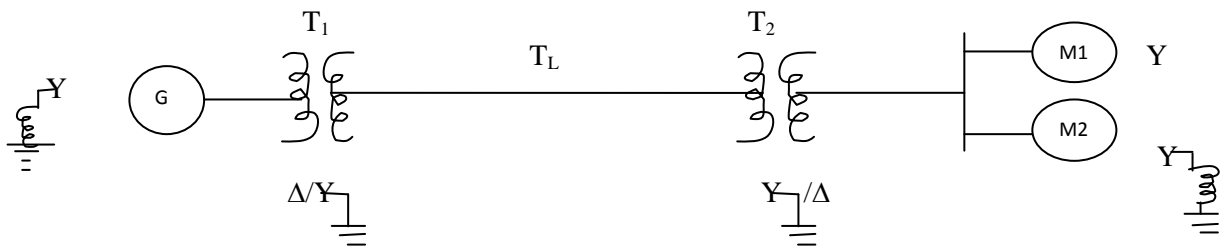- b) Draw the zero sequence reactance network. The current limiting reactor of 2.5Ω are connected in the neutral of motor no.2 & generator choose a box 25 MVA, 11KV in generator 07



- G: 25MVA, 11KV, 10%
 T₁: 30MVA, 10.8/121KV, 10%
 T₂: 30MVA, 121/10.8KV, 10%
 T_L: j300Ω
 M₁: 15MVA, 10KV, 25%
 M₂: 7.5 MVA, 10KV, 25% **For figure 4**

- Q.9 a) Derive the expression for fault current for L-L-G fault & draw the sequence network 08

- b) A 3phase, 37.5 MVA, 33KV, alternator having $x_1 = 0.18 p.u$, $x_2 = 0.12 p.u$ and $x_0 = 0.10 p.u$ based on its rating is connected to a 33Kv overhead line having $x_1 = 0.63 p.u$, $x_2 = 0.63 p.u$ and $x_0 = 0.126 pu$ A single line to ground fault occurs at the remote end of the line. The alternator neutral is solidly grounded. Calculate fault current in KA. 07

- Q.10 a) Explain the open conductor fault 07

- b) Explain the contingency analysis for security 08