

Total No. of Printed Pages:1

**SUBJECT CODE NO: E-89**  
**FACULTY OF ENGINEERING AND TECHNOLOGY**  
**F.E.(All) (CGPA) Examination Nov/Dec 2017**  
**Basic Electronics Engineering**  
**(REVISED)**

[Time: 2:00 Hours]

[Max.Marks:40]

Please check whether you have got the right question paper.

- N.B
- i. Q.No.1 is compulsory
  - ii. Solve any two questions from remaining questions
  - iii. Assume suitable data whatever necessary.
- Q.1 Solve any five. 10
- a) Enlist Different types of resistors
  - b) Draw the symbols of NPN Transistor & TRIAC.
  - c) Define Rectifier
  - d) State any two Boolean laws
  - e) Write Colour code for the following
    - i)  $240\Omega, \pm 20\%$  ii)  $1\Omega, \pm 5\%$
  - f) Define Latching current
  - g) Draw circuit diagram of half wave rectifier
  - h) Write 1's complement of the following
    - i.  $(100001)_2$  ii.  $(110011)_2$
- Q.2 08
- a) What are the different types of capacitor? Explain any one in detail.
  - b) Explain construction, working & principle of TRIAC device. 07
- Q.3 07
- a) What is need of rectifier? Explain bridge rectifier with circuit diagram.
  - b) Explain Adjustable voltage regulator using LM317. 08
- Q.4 07
- a) Implement NOT, OR & AND Gate by using NAND gate.
  - b) Perform following conversion. 08
    - i.  $(347)_8 = ( )_2 = ( )_{16}$
    - ii.  $(100001)_2 = ( )_{10} = ( )_{16}$
- Q.5 Write short note on (any three) 15
- a) DE-MORGANS Theorem
  - b) SCR
  - c) Zener diode as voltage regulator
  - d) 1'S complement & 2'S complement
  - e) Voltage regulator IC 78XX & IC 79XX

2017