

Subject Code : 247

FACULTY OF ENGINEERING & TECHNOLOGY
F.E. (All) (Old) Examination
NOVEMBER/DECEMBER, 2017

Elements of Electrical Engineering

Time: Two Hours

Max. Marks: 40

“Please check whether you have got the right the question paper”

- Note:
- Q. No. 1 is compulsory.
 - Solve any two question from question no 2 to 5
 - Assume suitable data if required

Q.1 Solve any Five from the following 2x5=10


- What is difference between self induced emf and mutually induced emf.
- What are the factors affecting the value of self inductance 'L'?
- State the effect of temperature on plastic and copper.
- Define reluctance.
- Define permeability.
- Define superposition theorem
- Define resistivity and state its expression.
- State 'Maximum Power Transfer' theorem

Q.2 (a) Derive the Discharging equation of the capacitor 05


(b) State and explain with neat diagram mutually induced e.m.f. 05

(c) Prove; $\alpha_2 = \frac{\alpha_1}{1 + \alpha_1(t_2 - t_1)}$ 05

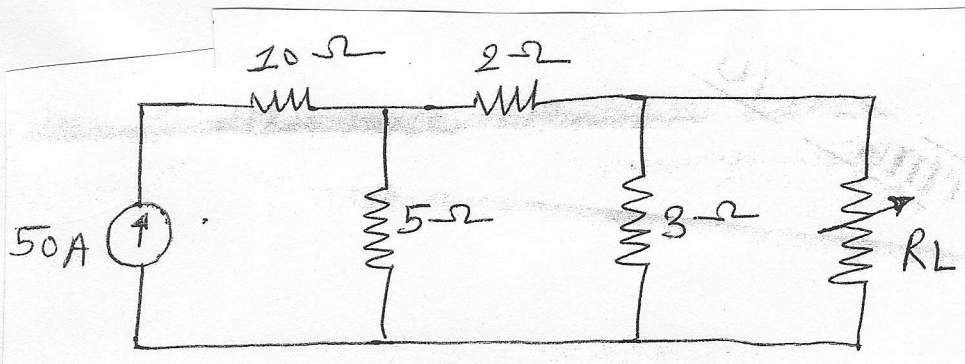Q.3 (a) Determine the 'maximum power delivered to the load in the circuit shown in figure. 05



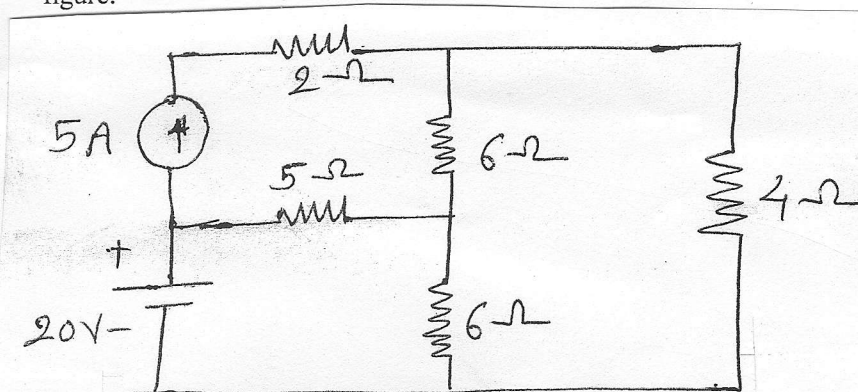(b) Use 'superposition theorem' find current in 4Ω resistance of show in figure. 05




P.T.O.

E - 2017

Subject Code : 247

-2-

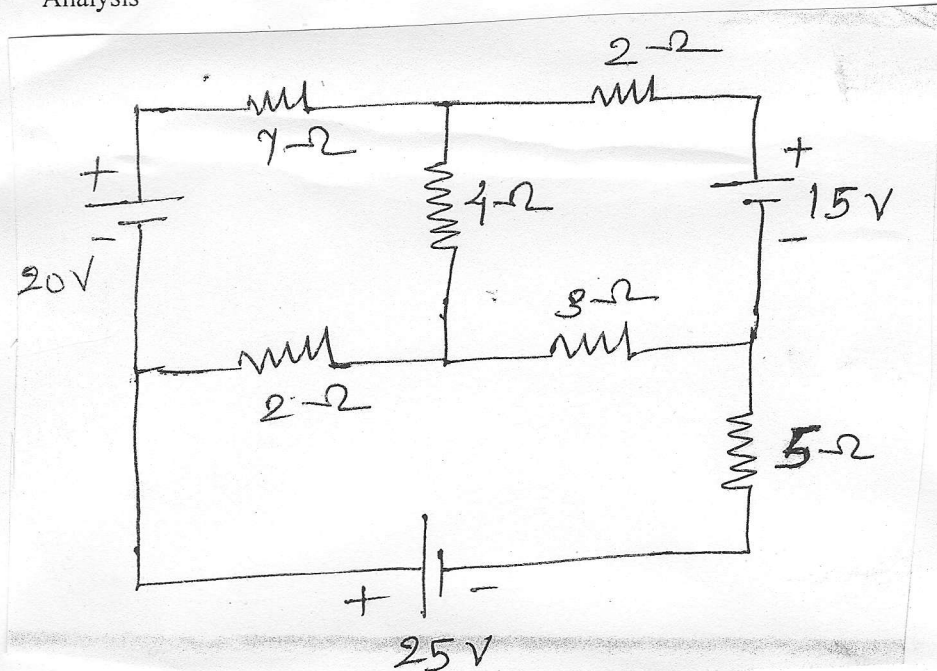- Q.3 (c) State and Explain 'Thevenin theorem' 05
- Q.4 (a) Comparison between Electric and Magnetic Circuit 05
- (b) Find the current flowing through '4' Ω resistance by using Mesh or Loop Analysis 05



- (c) A coil of 200 turns and resistance of '20' Ω is wound uniformly on an iron ring of mean circumference 50 cm and cross sectional area 4 cm². It is connected to 24V d.c. supply ($\mu_p = 800$) 05
- Find :
- i) MMF
 - ii) Magnetising force
 - iii) Total flux
 - iv) Reluctance
- Q.5 (a) State and Explain Eddy current loss
- (b) State and explain hysteresis loss
- (c) State and explain magnetic fringing and magnetic leakage.
