[Total No. of Printed Pages:2]

CODE NO:- Z-079

FACULTY OF ENGINEERING

F.E Year Examination - June– 2015 Elements of Electrical Engineering

(Revised)

[Time: Two Hours]

[Max. Marks: 40]

10

05

05

05

05

"Please check whether you have got the right question paper."

- i) Question. No. 1 is compulsory.
- ii) Attempt any two questions from remaining questions
- iii) Assume suitable data if necessary
- iv) Figures to the right indicate full marks


Q.1 Solve <u>any five</u> questions

1) State the factors affecting the value of resistance. State the effect of temperature on resistance of 1) gold 2) Rubber

2) Define RTC. Prove,
$$\alpha_o = \frac{Rt - R_o}{R_o t}$$

- 3) Define self inductance and mutual inductance
- 4) Write the equations for current and voltage during discharging. Draw the curves w.r.t. time
- 5) Define MMF, magnetic flux, Reluctance
- 6) Give four similarities between magnetic and electric circuits
- 7) State superposition theorem
- 8) Define time constant of charging circuit

Q.2 a

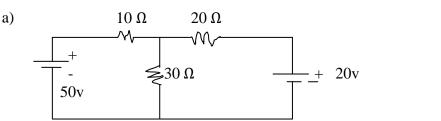

Find current through 30Ω resistance using Thevenin's theorem.


b) 2Ω 1.5A $\leq 4 \Omega \leq 5\Omega$

Find current through 5Ω resistance using superposition theorem

8v

c) State and explain maximum power transfer theorem

Q.3

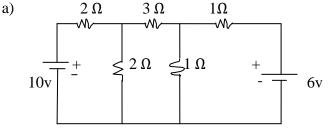

Find current through 3Ω resistance using Loop analysis

	b)	$+$ $4 0^{\text{M}}$ 3^{M}	05
		$6v - \boxed{ + 12 } = 5\Omega $ $+ 12 $	
		Find current through 5 Ω using Nodal analysis	
	c)	State and explain Thevenin's theorem	05
Q.4	a)	Define R.T.C state, it's unit. if α_1 and α_2 are R.T.C. at $t_1^0 c$ and $t_2^0 c$ respectively then prove $\alpha_2 = \frac{\alpha_1}{1 + \alpha_1(t_2 - t_1)}$	05
	b)	State and explain in brief the concept of self induction	05
	c)	With neat ckt diag and waveforms explain the charging process of capacitor. Derive the equations for charging voltage, current & charge	05
Q.5	a)	Give the comparison of electric and magnetic circuit	05
	b)	Explain hysteresis and eddy current loss	05
	c)	A mild steel ring of 30cm mean circumference has a cross sectional area of 6cm^2 is wound by a 500 turns coil. The ring is cut with 1mm air gap 4A current in the winding produces flux density of 1T in	05

turns coil. The ring is cut with 1mm air gap. 4A current in the winding produces flux density of 1T in the air gap. Find relative permeability of mild steel neglect leakage 'fringing'